Table 1: Power Amplifier Performance Summary Table K.R.Srinivas EE18B136

	Design Metric	Performance	Specification
Output P1dB	fo = 1.9 GHz	10.193 dBm	≥ 10 dBm
	$f_0 = 2.0 \text{ GHz}$	10.324 dBm	≥ 10 dBm
	fo = 2.1 GHz	10.605 dBm	≥ 10 dBm
AM-PM	fo = 1.9 GHz	5.4°	≤ 5 degrees
deviation at	$f_0 = 2.0 \text{ GHz}$	5.3°	≤ 5 degrees
P1dB	fo = 2.1 GHz	5.25°	≤ 5 degrees
Voltage-gain	fo = 1.9 GHz	2.50	≥ 2
from gate to	$f_{O} = 2.0 \text{ GHz}$	2.53	≥ 2
drain	$f_{O} = 2.1 \text{ GHz}$	2.56	≥ 2
Power	PA average power consumption [Excluding Bias]	35.78 mW	-
	Bias circuit power consumption	0.60 mW	Minimize
Other	Sum of all capacitances [Including AC coupling]	20 nF	-
	Inductance used	5 nH	-
	Simulator Used	Eldo	-