 


## DESIGN PROCEDURE & CHALLENGES :

### TOPOLOGY :



### PROCEDURE :

We start with the above topology of “ Common-Source Power Amplifier with Inductive Load”

- Given  $R_L = 50\Omega$  and minimum  $P_{out}$  delivered is 10mW (10dBm), we calculate the minimum voltage swing at the node X and  $I_{rms}$  required.

$$P_{out} = V_s^2 / 2R_L, \Rightarrow V_s (\text{amplitude voltage swing at X}) = 1V, \text{ which allows a } V_{d,sat} = 0.2 V.$$

$P_{out} = I_{rms}^2 R_L, \Rightarrow I_s (\text{amplitude current swing at X}) = 20mA$ , which allows  $I_{bias} = 20mA$  (to satisfy cut-off requirement). Since the voltage swing required at output is reasonable and within  $V_{dd}$ , we don't require any matching network to tune down the load resistance seen by the drain of transistor.

Assuming the length of the MOSFET to be 120nm, we can proceed to compute  $W$  of the transistor.  $I_{bias} = 0.5 * \mu_n C_{ox} W/L * V_{d,sat}^2$ , which gives  $W = 80\mu m$ . The bias inductor  $L_{bias}$  is set to 4nH .

- For the assumed values of parameters the  $P_{out}$  is fairly satisfied. To improve Gain, we increase  $W$  and  $I_{bias}$  proportionately and tune  $L_{bias}$  to check on AM-PM deviation. We finally arrive at  $W = 120\mu m$ ,  $I_{bias} = 25mA$ ,  $L_{bias} = 5nH$

### CHALLENGES :

- My phase deviation in AM-PM characteristic slightly exceeds the given specs, but I am unable to fix it anything better. Not sure about the reason.

**Note :** I'm not explicitly attaching hand calculations as I have mentioned clearly how to arrive at basic parameters in the first paragraph of design procedure.